

GOOD ANTENNAS TERRIBLE MEASUREMENTS


By Melvin C Vye W8MV

w8mv@arrl.net

September, 2020


BASIC CONCEPT #1

CONSERVATION OF ENERGY (POWER)

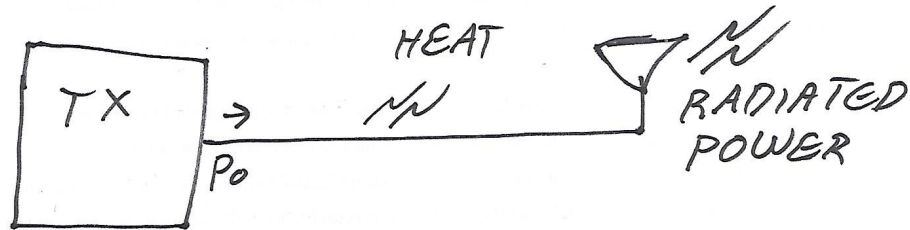

BASIC CONCEPT #2

MAX POWER OUT

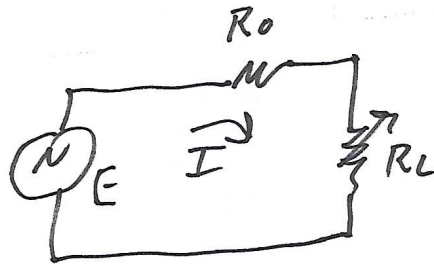

MAX POWER IN
LOAD WHEN
 $R_L = R_0$

$$I = \frac{E}{R_0 + R_L} \quad I^2 = \frac{E^2}{(R_0 + R_L)^2} = \frac{E^2}{R_0^2 + 2R_0R_L + R_L^2}$$

$$P_L = I^2 R_L = \frac{E^2 R_L}{R_0^2 + 2R_0R_L + R_L^2}$$

$$\frac{dP_L}{dR_L} = \frac{(R_0^2 + 2R_0R_L + R_L^2)E^2 - E^2 R_0(2R_0 + 2R_L)}{(R_0 + R_L)^4}$$


$$\frac{dP_L}{dR_L} = 0 \Rightarrow E^2(R_0^2 + 2R_0R_L + R_L^2) = E^2 R_0(2R_0 + 2R_L)$$

$$R_0^2 + 2R_0R_L + R_L^2 = 2R_0R_L + 2R_L^2$$

$$R_0^2 + R_L^2 = 2R_L^2$$

$$R_0^2 = R_L^2$$



$$R_0 = R_L$$

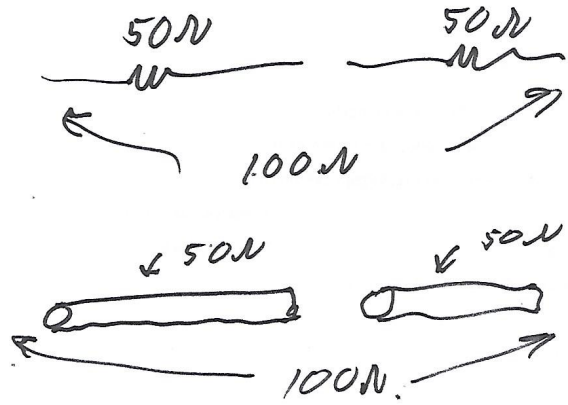


$$R = f(\epsilon, l) = \frac{\epsilon}{l}$$

$$Z_0 = f(\mu, \epsilon)$$

μ = PERMEABILITY ($\frac{H}{m}$)

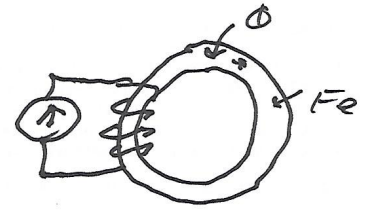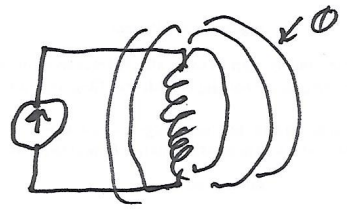

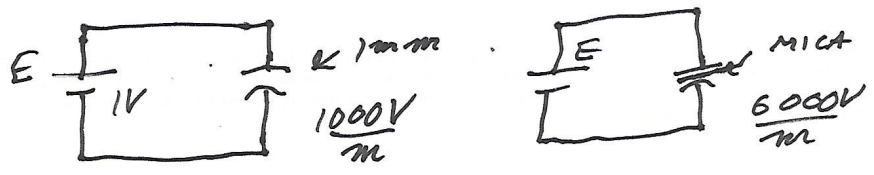$\epsilon = \text{PERMATIVITY } \left(\frac{F}{m}\right)$




$$Z_0 = f(\mu, \epsilon) = \sqrt{\mu/\epsilon} \left(\frac{H}{F}\right)$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_0^2 = \frac{1}{LC}$$


$$\omega_0^2 L^2 = \frac{L}{C} \quad (\Omega^2)$$

SO UNITS $\frac{H}{F} = \Omega^2$

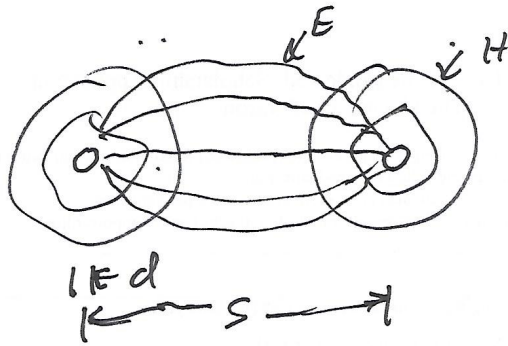

TWIN
LEAD
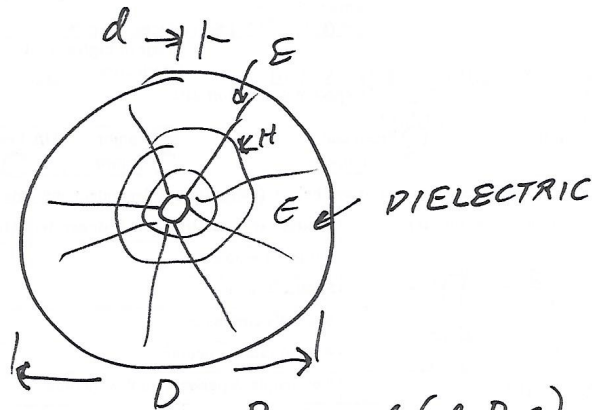
$$Z_0 = 276 \log \frac{2S}{d} \quad \text{TYP } \begin{matrix} 300\Omega \\ 450\Omega \\ 600\Omega \end{matrix}$$



COAX

$$Z_{0 \text{ AIR}} = 138 \log \frac{D}{d} = f(d, D, \epsilon)$$


TYP $\begin{matrix} 50\Omega \\ 75\Omega \end{matrix}$

$$Z_{0_{FS}} = \sqrt{\mu_0 / \epsilon_0}$$


$$= 377 \Omega$$

$$\mu_0 = 4\pi \times 10^{-7} \frac{H}{m}$$

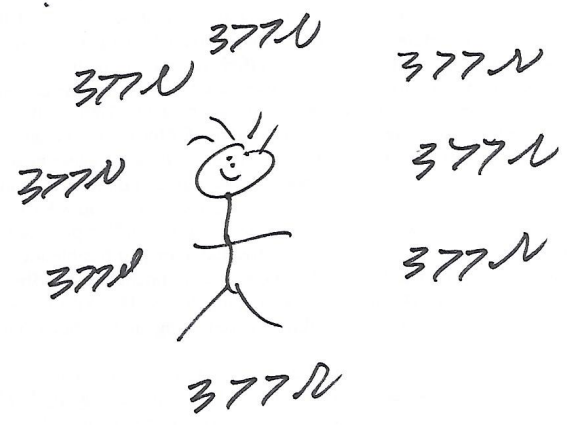
$$\epsilon_0 = 8.85 \times 10^{-12} \frac{F}{m}$$



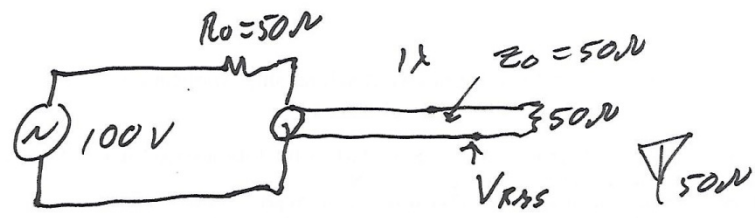SO ANTENNAS MATCH $Z_{0_{FS}}$ OF TL (50Ω)
 TO $Z_{0_{FS}}$ (377Ω)





$$V = I R = 50V$$

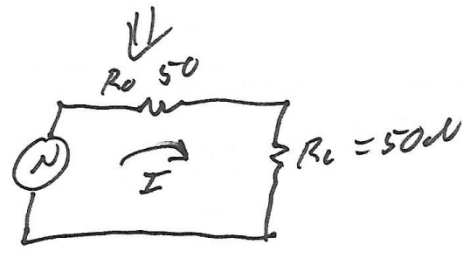

$$I = 1A$$

$$P = I^2 R = 50W$$

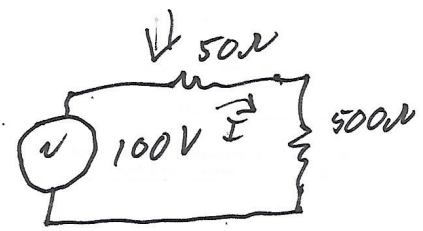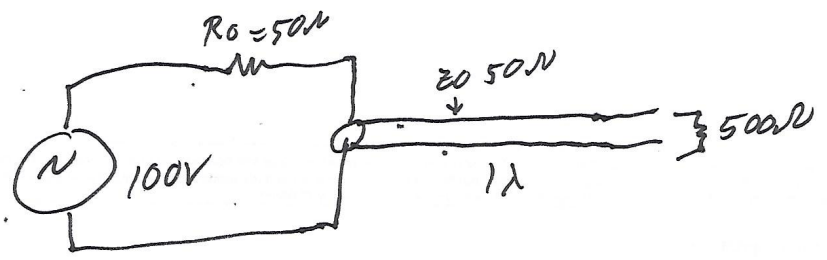

$$I = \frac{100V}{550\Omega} = 182 \text{ mA}$$

$$P = I^2 R = 16.5 \text{ W}$$

$$E_{MAX} = E_L = 100V \frac{500\Omega}{550\Omega} = 90.9V$$

$$P = \frac{R_L - Z_0}{R_L + Z_0} = \frac{450}{550} = 0.818 = \frac{E_R}{E_F}$$

$$E_R = 0.818 E_F$$

$$E_R + E_F = E_{MAX}$$

$$0.818 E_F + E_F = E_{MAX} = E_L$$

$$1.818 E_F = E_{MAX} = 90.9V$$

$$E_F = 50V \quad E_R = 40.8V$$

$$E_{MIN} = E_F - E_R = 50V - 40.8V = 9.2V$$

$$\frac{E_{MAX}}{E_{MIN}} = \frac{90.9V}{9.2V} = 10 = SWR = \frac{R_L}{Z_0}$$

$$\rho = \frac{E_R}{E_F}$$

$$\rho^2 = \frac{E_R^2}{E_F^2} = \frac{E_R^2 / \epsilon_0}{E_F^2 / \epsilon_0} = \left(\frac{P_R}{P_F} \right)^2$$

$$\rho = \sqrt{P_R / P_F}$$


$$P_L = P_F - P_R$$

$$P_R = \rho^2 P_F$$

$$P_L = P_F - \rho^2 P_F \\ = (1 - \rho^2) P_F$$




$$P_F = \frac{P_L}{1 - \rho^2} = \frac{16.5 \text{ W}}{1 - .818^2} = 50 \text{ W}$$
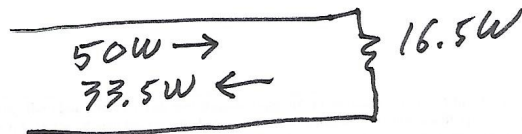
$$P_R = 50 \text{ W} - 16.5 \text{ W} = 33.5 \text{ W}$$



FIX IT!

10

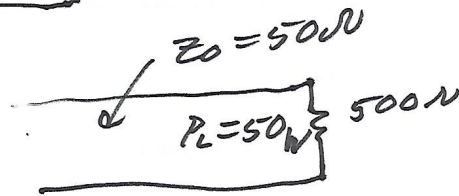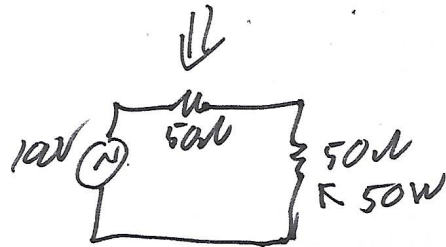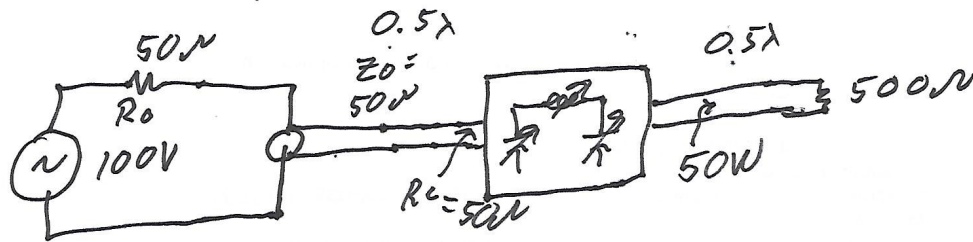

$$P_L = \frac{E_L^2}{R_L} \quad E_L = \sqrt{P_L R_L} = 158V$$

$$\rho = 0.818 = \frac{E_R}{E_F} \quad E_R = 0.818 E_F$$

$$E_R + E_F = 158V$$

$$0.818 E_F + E_F = 158V$$

$$1.818 E_F = 158V \quad E_F = 86.9V \quad E_R = 71.1$$

$$E_{MAX} = E_F + E_R = 158V$$

$$E_{MIN} = E_F - E_R = 15.8V$$

$$\frac{E_{MAX}}{E_{MIN}} = 10 = SWR$$

$$P = \sqrt{P_R / PF}$$

$$P_L = P_F - P_R$$


$$P^2 = P_R / PF$$

$$P_R = P^2 PF$$

$$P_L = P_F - P^2 PF$$

$$P_F = \frac{P_L}{1 - P^2} = \frac{50W}{1 - P^2} = 150W$$

$$P_R = 150W - 50W = 100W$$

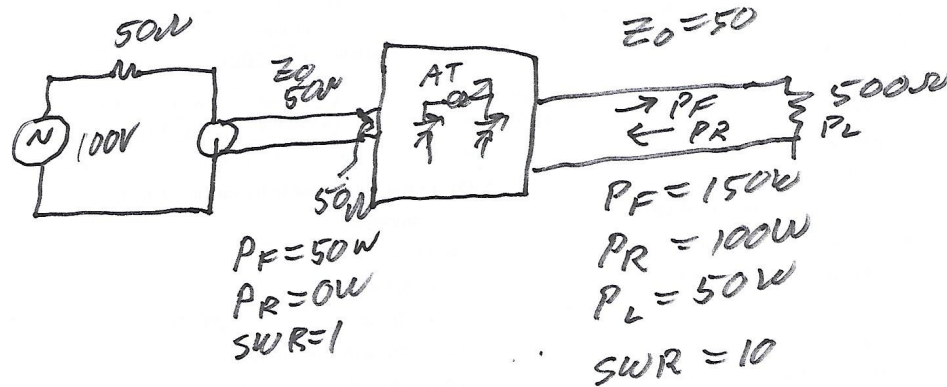

$$\rho = \frac{E_R}{E_F}$$

$$\begin{aligned} E_{MAX} &= E_F + E_R \\ &= \rho E_F + E_F \\ &= (1 + \rho) E_F \end{aligned}$$

$$\begin{aligned} E_{MIN} &= E_F - E_R \\ &= E_F - \rho E_F \\ &= (1 - \rho) E_F \end{aligned}$$

$$SWR = \frac{E_{MAX}}{E_{MIN}} = \frac{(1 + \rho) E_F}{(1 - \rho) E_F} = \frac{1 + \rho}{1 - \rho} = \frac{1 + \sqrt{P_R / PF}}{1 - \sqrt{P_R / PF}}$$



11 10028,126,110
EN90 23 130 2

Menu

Edit

QRP Labs

MFJ DELUXE VERSA TUNER II

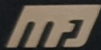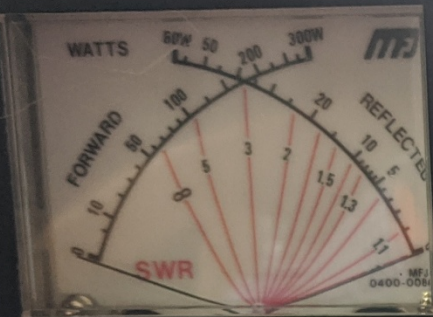

MODEL MFJ-949E

ANTENNA SELECTOR

TUNED **BYPASS**
COAX 2 COAX 2
COAX 1 COAX 1
BAL. LINE WIRE BAL. LINE WIRE
ON 300W PEAK
OFF 30W DUMMY LOAD DUMMY LOAD AVG
LAMP METER

TRANSMITTER MATCHING

0 1 2 3 4 5 6 7 8 9 10


INDUCTOR SELECTOR

L A B C
K J I H G F

ANTENNA MATCHING

0 1 2 3 4 5 6 7 8 9

VECTRONICS™

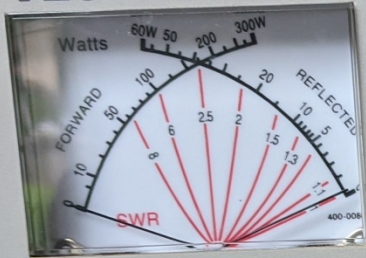

DIRECT — TUNED

COAX 2

COAX 1

COAX 1

COAX 2

BYPASS

WIRE/BAL

LAMP



ON
OFF

RANGE



3kW
300W


LEVEL

OFF

DELAY

INDUCTOR


SWR

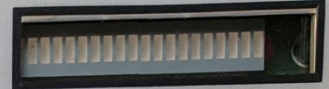

Peak Forward Power



ANTENNA

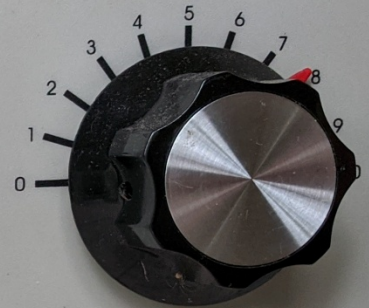

TRANSMITTER

Model HFT1500 Digital Peak Reading Antenna Tuner